

[\[Edit project log - Delete project log\]](#)

Open Collector FAIL. The ATX power-switch saga continues.

A project log for [Improbable Secret Project](#)
*Probability this can work: 98%, working well:
70%, working within 1k: 10%. A LOT of work,
and utterly ridiculous.*



[esot.eric](#) • 12/24/2016 at 03:21 • [27 Comments](#)

Update 1-16-17: It's NOT Friggin' Diodes! [AND I FOUND A USE!](#)

Update 1-15-17: FRIGGIN DIODES! (see the bottom)

Update II, vague recollection of BJTs used instead of diodes for reverse-polarity-protection. Notes and excessive ramblings at the end.


Update 1-2-17: Found some discussion about misuse of transistors, similar to what I experienced, here. Notes and ramblings and no conclusions added to the bottom.

In the interest of making this blasted thing even more robust, yahknow, by being in-spec, rather'n just "it works" and moving on... And, since I was already modifying the circuit to lower the pull-down resistor (see last log), and add a Power LED...

I decided to add a transistor to the output of the Flip-Flop. Thus, the connection to the

/PWR_ON signal would be open-collector, and capable of sinking more current, if necessary (e.g. on another Power Supply, should this one go flakey).

Simple!

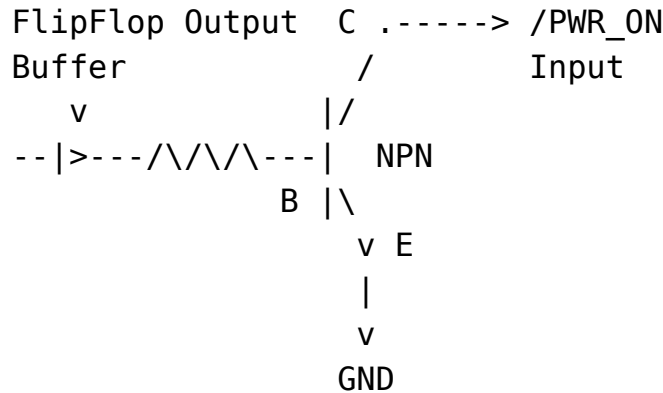

The /PWR_ON signal powers up the system when grounded, and the system is OFF when that pin is floating/unconnected. So, obviously, it must have a pull-up resistor somewhere in the circuit (if necessary).

I powered it up (works great! Finally!)

But the stupid LED wasn't lighting. Alright, musta reversed it... Swapped the polarity, and sure 'nough, it's lit. Excellent!

No, wait... WTF... The fan's not spinning. push the button and the LED goes off but the Fan starts up.

WTF?

....

The LED is connected to the Q (non-inverted) output of the FlipFlop, anode tied high through a resistor (since TTL has much greater drive-strength when driving low).

The /Q output drives the transistor when high.

(Note To Self: drive-strength??? hFE measured at 220... is that better than just driving low from the TTL output? Heh, barely... IOH <= 0.8mA, IOL <= 16mA. And, frankly, there's no way the /PWR_ON input could draw 16mA, right?)


So the LED should activate (cathode driven low) when the /Q output is high, which also drives

the transistor, pulling the /PWR_ON signal low, powering the system.

So... what's wrong now...?

Ultimately... Turns out I grabbed a PNP by mistake.

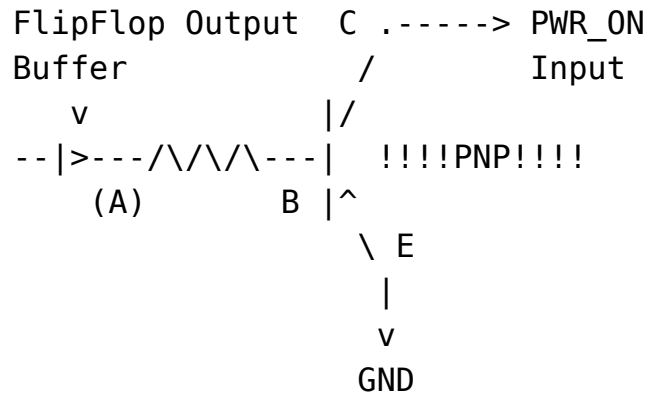But now I'm **really** confused. **How the heck can this thing work at all?!**



VBE will never be forward-biased!

Measurements (between point and GND):

SYSTEM OFF:

VA = 3.9V

VB = (not measured)

VC = 4.5V

(VE = 0.0V)

SYSTEM ON:

VA = 0.1V

VB = 0.2V

VC = 0.8V

(VE = 0.0V)

Alright, so, have we established, yet, that I'm certainly no BJT expert? This was mentioned in the last log, as well as a few logs on other projects (e.g. the Transistor-based RS-232 inverter, which wound up acting as an amplifier)...

But, here I think I can see something that *sort of* makes sense...


Note the voltage difference when ON: $V_C - V_B$ (VBC) = 0.6V... A transistor-bias voltage, if I've ever seen one... Except, VBC, not VBE.

And, similarly, when OFF: $V_C - V_A = 4.5 - 3.9 = 0.6V$... (Imagining not much drop across that resistor, since there's little current flowing between the Emitter and Collector.

But... WEIRD.

OK, I'm pretty sure I've read somewhere that swapping E for C will still function, but at a *really low* h_{FE} ... So I plug one in the ol' transistor-meter backwards, and sure-enough $h_{FE} = 2$ (when forward, $h_{FE} = 220$).

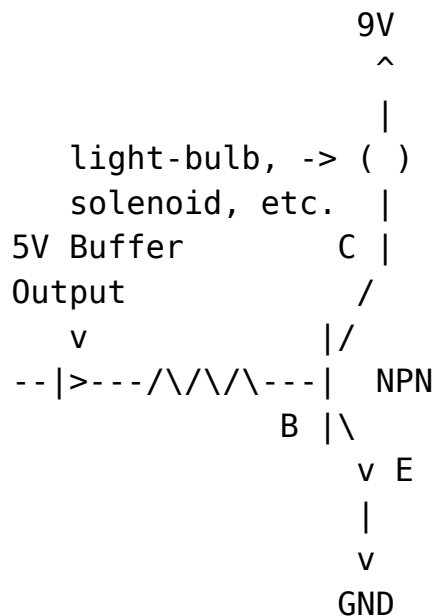But, I can't let this go... this just doesn't seem right to me. If you can turn on a transistor with VBC, then how come all those open-collector circuits don't turn themselves on...?




VBC is always greater than 0.6V, in this case... OK, so it's not the *voltage* that turns it on, but

the *current*, right? But, we've already seen that current through VBC can turn on the transistor... right?

So then, I guess, in this circuit IBE may be lower than IBC... And with hFE, it...

Oh, NO... In this case, VBC is $< -0.6V$. Reverse-Biased. OK.

But then what if you've got:

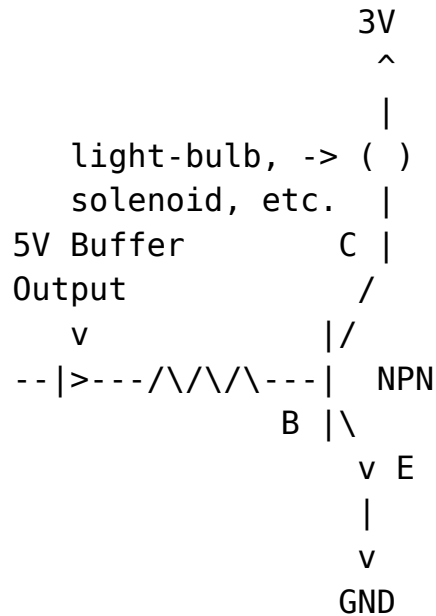

Ah, right, so... When the buffer outputs 5V, BOTH VBE and VBC are forward-biased, the switch turns on. Right. When the buffer outputs 0V, I guess we rely on the hFE to determine how "off" the transistor will be... because ... NO. VBC is reverse-biased, it'll inherently be off.

Man, once these things seemed so intuitive to me...

Lesson repeatedly-learned the hard way: **Transistors Are NOT Switches. They're more like Teeter-Totters.**


And... This is just another in the *LONG* list of things that should've been easy that have turned into *huge* ordeals prepping for *this* project, which *still* hasn't even started.

Found an interesting discussion kinda touching on my PNP-resistor experience...

<https://www.researchgate.net>

[/post/Can_we_reverse_a_BJT_by_injecting_the_input_current_into_the_collector_and_taking_the_base-emitter_voltage_as_an_output](#)

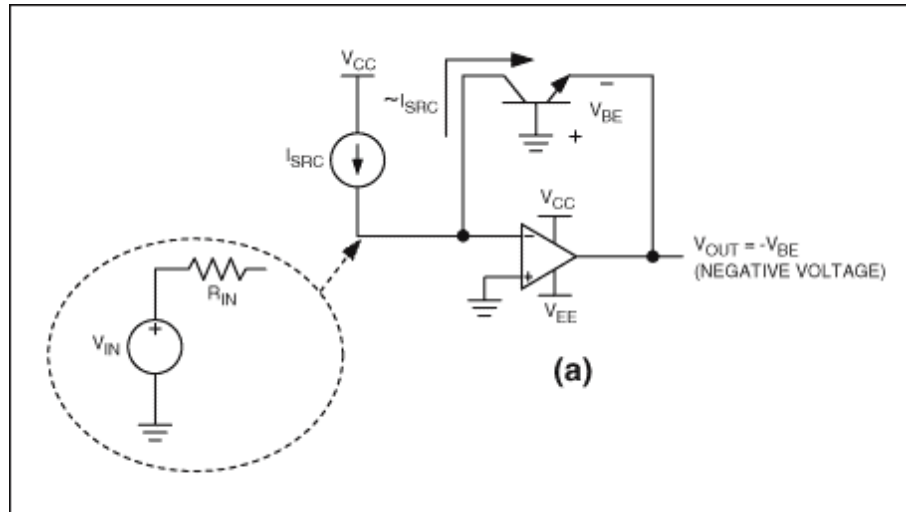And some really weird linking-system making it impossible to show the image here without my re-uploading it. Weeee: (not my work):



Except, actually, this one's a lot more obvious to me... In fact, it's pretty much normal BJT-biasing. In fact, it's not at all similar to my circuit, now that I look further. (V_{CE} is reverse-biased, V_{BE} is forward-biased like a regular-ol' BJT circuit). Though it's interesting, nonetheless.

Again, what I had was:

```

: 5V
: ^
: |
: /
: \ PRESUMED
7400-series *TTL* : /
FlipFlop          : |
Output            + C .->:>-+---|>---
Buffer            0.6V / : Gate(?)
v                - | / : .....
--|>---/\ /\ /\---| !!!!!PNP!!!!
(A)              B | ^
+ : + \ E

```

```

      :    0.2V |
0.1V : REVERSED v
-    :    -   GND

```

Measurements (between point and GND):

SYSTEM OFF:

$V_A = 3.9V$, $V_B =$ (not measured), $V_C = 4.5V$, ($V_E = 0.0V$)

SYSTEM ON:

$V_A = 0.1V$, $V_B = 0.2V$, $V_C = 0.8V$, ($V_E = 0.0V$)

So, when on, this is acting as a non-inverting *buffer* rather than the typical *inverter* I'd've experienced if this were the NPN I intended.


And, when on, I'm getting:


$V_{BE} = 0.1V$ (NOT enough to turn on the diode, nevermind being *reverse* biased for a PNP)

$V_{BC} = -0.6V$ (a diode-drop... also properly-biased for a PNP)

And... random-observation: *exactly* the output-voltage a regular ol' TTL considers V_{IL-Max} . (Hmmm). Some discussion I read, either at that link, or another it linked, suggests that TTL actually used this design(?).

So, plausibly, if I hadn't done this with a regular ol' TTL 7400-series chip, and instead used CMOS or something of this era, this wouldn'ta worked, since the drive-strength and voltage of the output, when high, would probably be enough to assure even V_{BC} would be zero, rather'n forward-biased... unless, somehow, ... nah, plausibly even "weirder" than that... if the output driving the base is *only* tied-high (when high), then no current could flow, the transistor would never turn on. Huh...

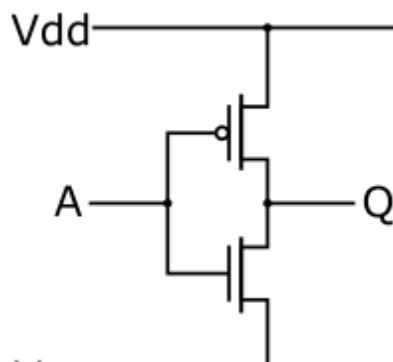


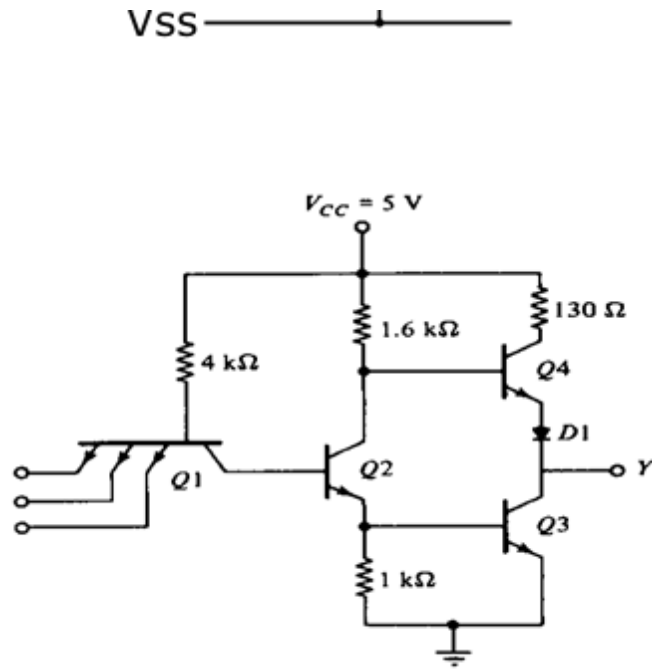

See, Q3 and Q4 can both be on simultaneously, depending on the load. But in the MOSFET case...? Hmmmm...

So many oddities!

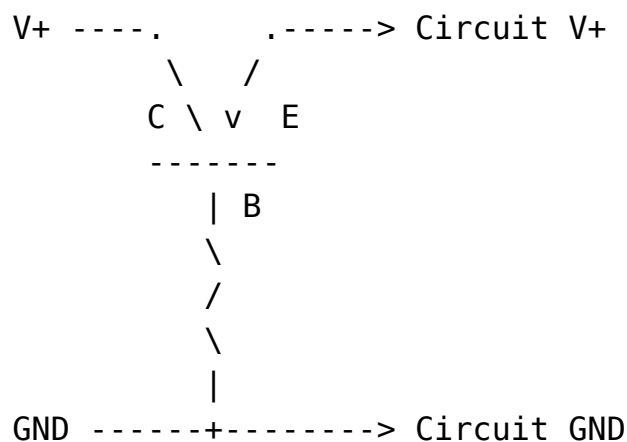
It's finally come back to me: Somewhere 'round this site, a year+ish ago, somehow it came up to use a BJT instead of a diode to protect a circuit from reverse-polarity...



(From Memory)

Yep. That's with the emitter connected to the LOAD, and V+ connected to the collector.

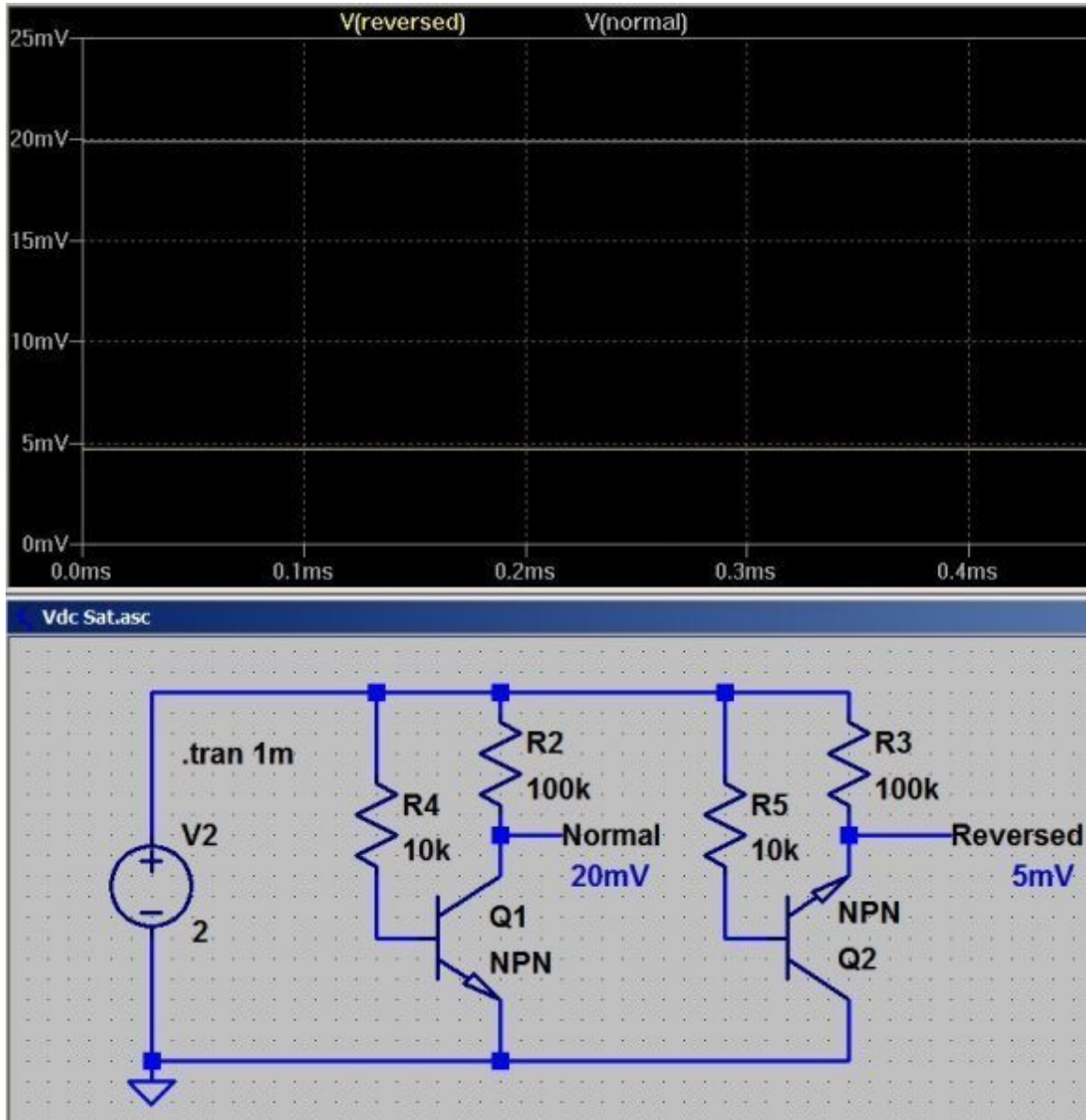
This guy turns on when VBC (not VBE) is forward-biased. As I recall, the purpose is that VEC is typically *smaller* than VCE. And an experiment [here](#) states the same. (Something like 1/4!)



Unlike my circuit, VBE will *also* be forward-biased in both of these circuits, but less-so than a full diode-drop.

So, I've still no idea what this thing I've run into could be useful for.. I had *an* idea, then started realizing all the inherent oddities I keep running into with various circuit elements' not working the way I'm used to.

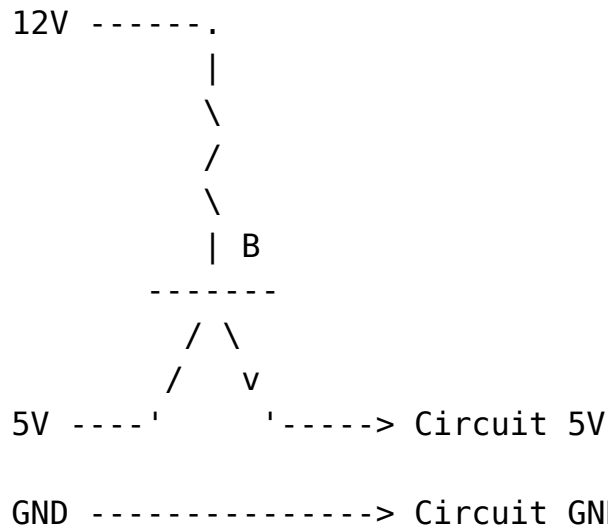So, one idea is similar to the reverse-polarity protection, except with an NPN instead of PNP.



A bit ridiculous, because it requires your 12V to be correctly-polarized... But, maybe, it could be used with/as e.g. a power-switch for some ridiculous reason...

BEWARE: I found out the hard-way... This will **NOT** work if you use a linear voltage-regulator to output that 5V (maybe from the 12V rail?).

Why...? Because, at the fundamental-level, of the same friggin' principle that got me into this mess in the first place, I think. Linear voltage-regulators are designed to **source** current, not to **sink** it, so, when the load's too small, this circuit would pull the 5V "regulated" output up to around 12V. HAHAHA.

A more obvious alternative is to do the same reverse-polarity circuit as earlier, except with an NPN on ground. But, yahknow, switching ground isn't such a great idea.

And, again, don't forget that h_{FE} is something like 2 (not 200) when turning on with VBC, so... if the circuit uses 1A, does that mean this thing would require 0.5A into the base? But, then, maybe that's irrelevant, because, again, once the circuit turns on, **both** VBC and VBE will be forward-biased... no, wait, forward-biased, but VBE's not going to reach the diode voltage-drop, so not **on**, right? No, wait... LOL this is ridiculous.


VBC will be, say, 0.6V, then VBE will be 0.595V! So, then... does that mean **both** sides are active, and h_{FE} is something like the average of 200 (C->E) and 5 (E->C) ?

This is **SO WEIRD**. 'Spose I should just dig out the ol' text-book and refresh myself. But apparently I'm in a rambling mood.

Anyways, it's not so much that I want to find *a use* for this thing (though that's always nice), but that I'm almost certain there must be somewhat common cases where this situation is actually an oft-neglected side-effect... Just can't seem to think of one.

UPDATE: DIODES:

Hah, I have no idea how I didn't see it before... the circuit's basically nothing more than diodes... (Oh, and I came up with a groovy AND gate from 'em... over at [#Random Ridiculousities and Experiments](https://hackaday.io/project/8348-random-ridiculousities-and-experiments/log/51939-transistor-oddities): <https://hackaday.io/project/8348-random-ridiculousities-and-experiments/log/51939-transistor-oddities>).

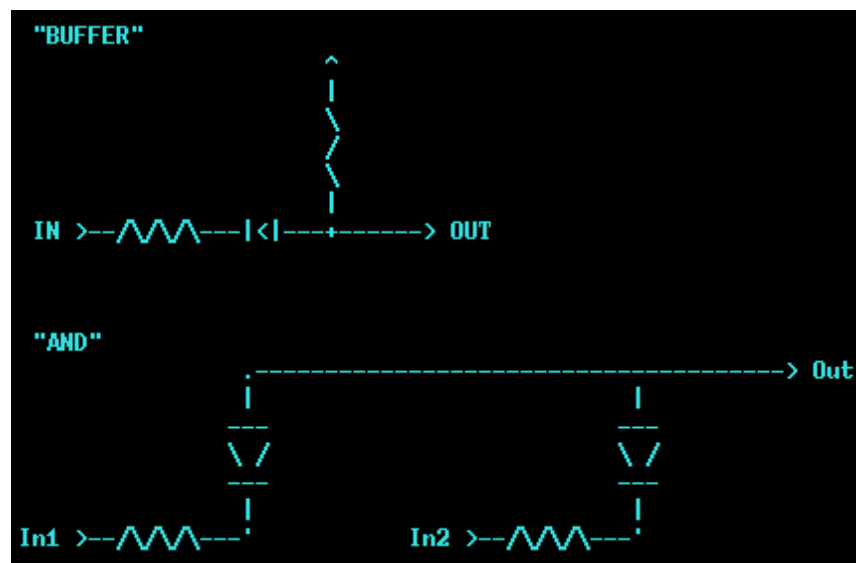

So, it's *slightly* better than using diodes... about twice. Since I measured the reverse-hFE as 2.

Previous Log

Casing + TTL-fail.

12/23/2016 at 22:35 • 0 comments

Next Log

It Has Begun!

12/30/2016 at 12:09 • 0 comments

DISCUSSIONS

Add your comment

Post comment



esot.eric wrote 01/08/2017 at 11:40

And there it is:

<https://www.computer.org/csdl/proceedings/afips/1958/5052/00/50520022.pdf>

Direct-Coupled Transistor Logic. Go @Yann Guidon / YGDES for laying out the breadcrumbs, but ultimately it was "Reverse Active Region" that got me there.

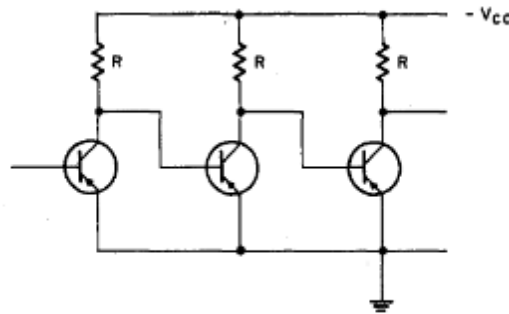


Fig. 1. DCTL inverters

reply edit delete



esot.eric wrote 01/08/2017 at 12:15

WRONG AGAIN! From every *other* source I can find on the matter, DCTL is, in fact, normally-biased... Those arrows point in the wrong direction.

Further, from "my circuit", these wouldn't be inverters, but *buffers*.

Sheesh, this whole endeavor is absurd.

reply edit delete



esot.eric wrote 01/08/2017 at 13:09

THE FRIGGIN' SAGA CONTINUES! Note the upper rail is NEGATIVE. I almost got sucked in when it explicitly stated "p-n-p"... Then I read "VBE" and thought "WTF?!" ... and finally, that is in fact -VCC. With a big ol' negative symbol before it. And all timing-diagrams show 0V as high, and



Yann Gourdon / YGDES wrote 01/08/2017 at 12:45

This is one *weird* adventure to say the least, describing Seymour Cray's reference around 1960. I use it to say in my book, CDC6600:
edit delete

http://ygdes.com/CDC/DesignOfAComputer_CDC6600.pdf

Enjoy !

reply



esot.eric wrote 01/08/2017 at 13:21

grumble dagnabbed Common-Emitter inverter-switches *grumble*.

This book looks like a great read, but if I ever sit down to read something greater than 20 pages, I'd better start with my dad's book. At least with search-fu, one can blame reading 100 pages on rabbit-holes or fractal-branches, or something...

edit delete



esot.eric wrote 01/08/2017 at 13:28

Then again "my circuit" *couldn't* be used (directly/explicitly) for logic... since it is a *buffer* not an inverter. Done and done. Guitar-pedals it is!

edit delete



esot.eric wrote 01/08/2017 at 10:46

"Reverse Active Region" ah hah. Search-fu is *significantly* improved with that term.

reply edit delete



esot.eric wrote 01/08/2017 at 10:55

Am I the only one who sees this as ironic...?

[PDF] [Lecture 18 - MIT](#)

web.mit.edu/6.012/www/SP07-L18.pdf ▼

6.012 Spring 2007. Lecture 18. 2. 1. BJT: Regions of Operation. • Forward active: device has high voltage gain and high β ; • Reverse active: poor β ; not useful;

Didn't we just discover that it's used in almost every TTL IC? or am I still mistaken in my understanding...?

reply edit delete



Yann Guidon / YGDES wrote 01/08/2017 at 11:11 • 1 point

not useful, but it always depends :-D

For example I have used BOTH the parasitic capacitance and the bulk diode for the discrete 10TFF cell :-D



Ted Yapo wrote 01/08/2017 at 16:18 • 1 point

I have a copy of Phil Hobbs' Building Electro-optical Systems, and in it (14.6.6) he says that inverted transistors are useful because they have very low saturation voltages ($\sim 10\text{mV}$), even though they have very low beta (2-5).

So, you might be able to substitute reversed garden-variety transistors for more expensive low- $V_{ce(sat)}$ devices in some cases.

(link to the book, not the passage)

<https://www.amazon.com/Building-Electro-Optical-Systems-Making-Work/dp/0470402296>



esot.eric wrote 01/09/2017 at 09:27

@Ted Yapo Good call re low saturation-voltage. I've seen that mentioned, as well.

Still trying to think of potential uses... With a beta of 2, obviously it's not much of an amplifier. And, at least in my configuration, it's a **buffer** not an inverter, so can't be used for logic-building-blocks...

Best I've got so far is an interface between high-current CMOS output (say $V_{ol-max}=1\text{V}$) level-shifting with large fanout to TTL at $<0.8\text{V}$... non-inverted ;)

That book is \$112 TO RENT! ;)

[edit](#) [delete](#)



Ted Yapo wrote 01/09/2017 at 17:51 • 1 point


Yep, it's an expensive book, but most of the stuff in there is hard-won practical info that usually never makes it out of the lab. Unless you're lucky enough to work with/for someone with that kind of experience, it would take a whole career or more to stumble into it on your own.



Maybe with the low β property of the reversed BJT, you could make a current mirror with compliance down to the mV range? The And here's someone claiming to use the reverse-active region as a guitar-effect... which apparently has interesting characteristics when clipping. should still be proportional.

Though, I don't see how this isn't just an emitter-follower, even though the author claims "obviously it is not".

<http://www.muzique.com/lab/reverse.htm>

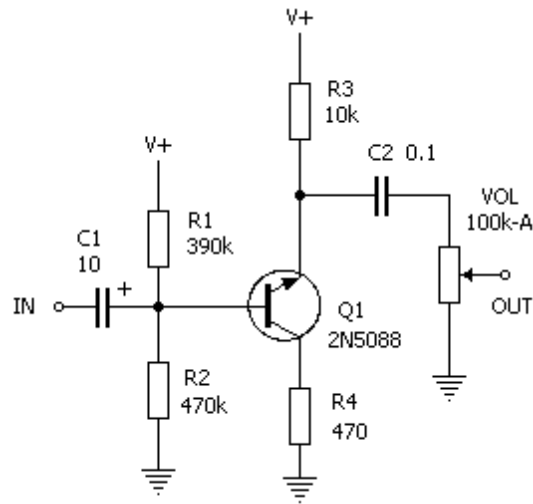

reply edit delete



Yann Guidon / YGDES wrote 01/08/2017 at 09:01

Just one question : did you finally succeed turning the ATX power on ?

reply




esot.eric wrote 01/08/2017 at 09:51

LOL. Yes. I think it's in the next log, maybe I forgot.

It *does* turn on, with this weird circuit, that's the weird part!

Well, *did*... I shoulda just left it, and changed the LED, 'cause it seemed reliable, and more importantly was such a weird circuit that I shoulda kept it running. But in the interest of having it "right" I changed it back to the regular ol' NPN "switch"/inverter.

reply edit delete

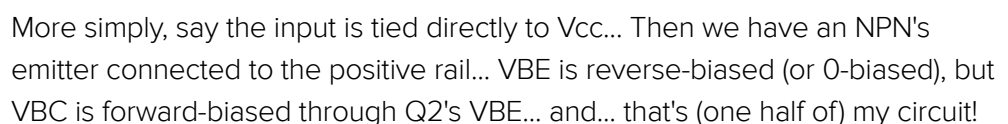



^ v

<http://www.righto.com/2017/01/die-photos-and-reverse-engineering.html>

ted raps wrote 01/07/2017 at 14:38


From the HxD blog

Here's another one to ponder:

<http://hackaday.com/2017/01/07/low-voltage-bjt-inverter/>

(Thank

reply

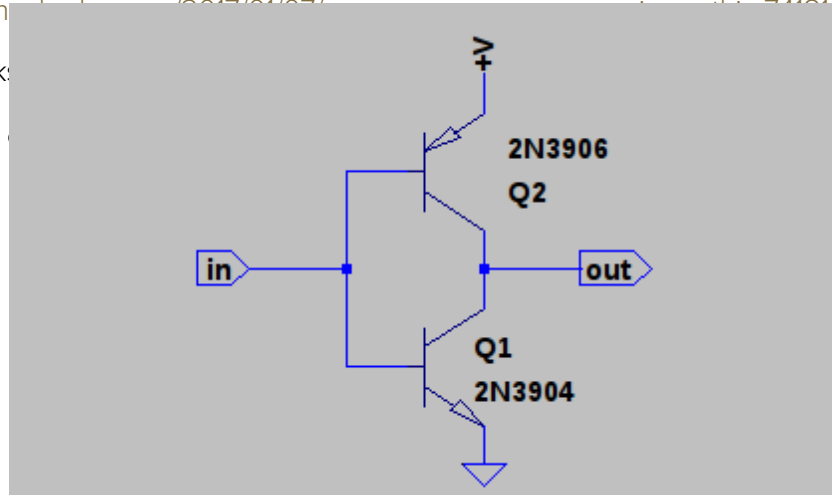

At first, you might think it's a pair of emitter followers, which you see this way all the time. But, no, it's a pair of common emitter "switches." If you apply more than about 1.4V of supply voltage, the pair just bias each other fully on, and quickly overheat (or worse), which is why you never see them hooked this way. But what about using a supply less than 1.4V? Now, the pair behaves like a CMOS inverter!

The allowable voltage supply varies with the transistor V_{be} , which is a function of temperature - it has to be above V_{be} but below $2 \cdot V_{be}$. So, you might need to adjust the supply with ambient temperature to make this usable, but I've wondered if you could make low-voltage BJT logic this way...

reply



esot.eric wrote 01/08/2017 at 01:33

Beware of utter rambling and likely point-missing :)


Uh huh! That common-emitter-switch idea was the basis of my first H-Bridge 20ish years ago... Took many a clever internet-folk to inform me of why they'd *both* be on simultaneously, and to insert a third transistor between the two bases.

But you're saying... use $V+$ less than $V_{BE} \cdot 2$... Interesting concept. Then it would work as I once naively thought; the common-emitter-switch idea




would've worked.
ed Rapo wrote 01/08/2017 at 15:46

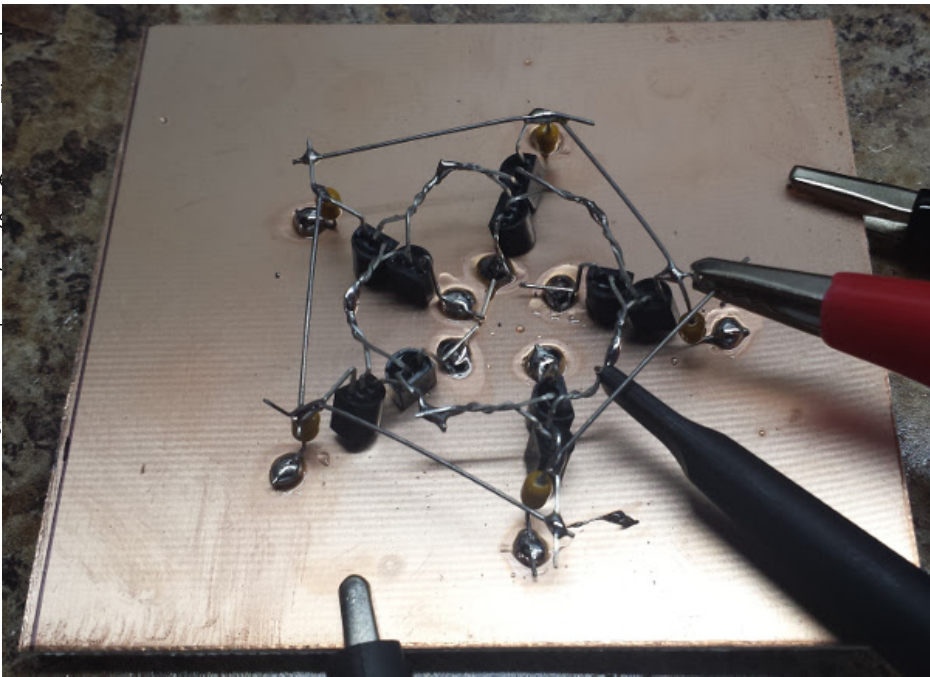Seems reasonable you could use this for low-voltage BJ logic. And coupled them into a ring oscillator - in the shape of a ring ;) Lots to ponder, in there...



They're 2N3904/2N3906 pairs. The capacitors are just supply bypass caps (0.47 uF each). The circuit seems to be "alive" down to about 0.4V, although very touchy and unstable. By 0.8V it shows nice, stable oscillations.
The PNP and NPN would be swapped... PNP at the bottom.

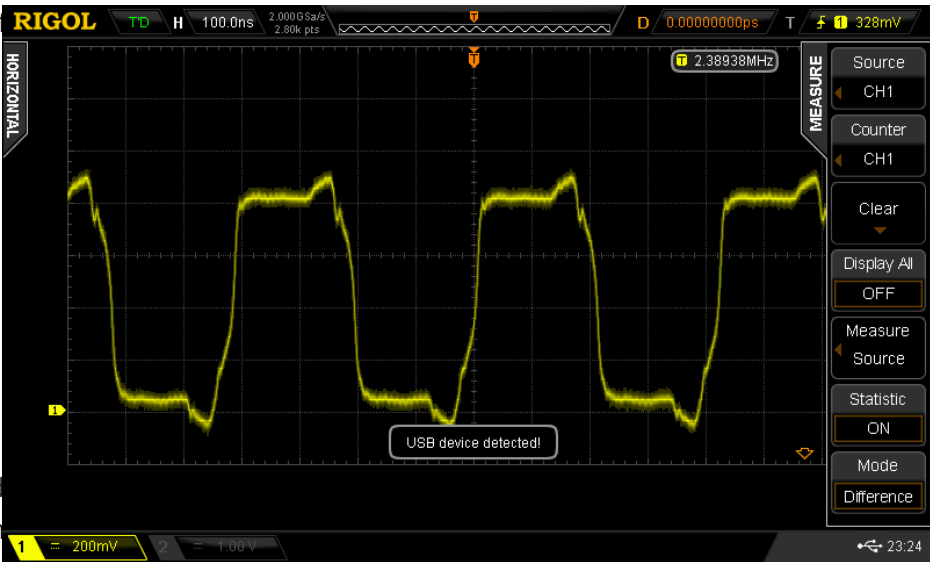

At 2.4 MHz (approx), this is a period of 420 ns, which I think you divide by 10 to estimate the propagation delay - 42ns. (Or do you divide by 5, I



^ v



^ v




^ v

So going back to my original circuit, anyway, they work as inverters, and produce a half-decent waveform. At 0.8V, it consumes about 30mA. By 1V, it was up to 100mA, but I didn't measure the oscillation frequency.

The 2N3904 has an FT of 250 MHz or so. The fastest pairs I have are MPSH10/MPSH81 (obsolete, I think) at 650 MHz. I wonder how they would do?

Yann Guidon / YGDES wrote 01/08/2017 at 17:38

It's up at #CBJT Logic :-D

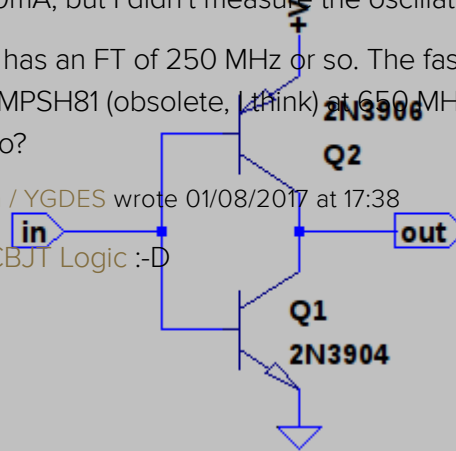

Yann Guidon / YGDES wrote 01/08/2017 at 09:18

And comparing it to mine... and looking only at Q1, for now:

@Ted Yap: Unusual logic gates : I'm very interested :-D

If the output voltage was *lower* than 0V (maybe pulled to -V through a resistor?), and the input voltage was higher than that by $V_{BE} = 0.6V$, you need as many PNP as NPN and it's harder to wire them in series (parallel but still lower than 0V, we'd have my circuit again... switching seems preferred, favoring ORs over ANDs but it should be tested).

...except that by the input being lower than V_{BE} , it turns on Q2, which

would pull the output high, which would "dissatisfy" (or override) the "collector-follower" nature of Q1... This is something I should investigate for #YGREC-Si, given that I have a good supply of both polarities ! Maybe this uses less transistors than ECL or output near V^+ ... and, yeah, then we're back to my circuit being a really weird case that I still have yet to be able to find described anywhere as anything more than a tiny side-note, let alone having a name.

Too bad I can't find a significant amount of NPN in Germanium... I must stick to classic ECL for #Germanium ECL. The lower threshold voltage would save some power but the leaks are just too significant. Let it be known, the circuit I've "discovered" is hereby called an esot-follower. And in 100 years when we've finally discovered a use for it in flying EM-drives, y'all will have to use my name to refer to it :)

_____reply

Alright, back to the low-voltage BJT logic.

Yann Guidon / YGDES wrote 01/08/2017 at 09:28

Not very likely V_{BE-on} will drop too much lower than 0.6V with temperature changes. What, maybe 0.4V at an extreme? So maybe somewhat reliably you could do 0.8V logic? Nice... Run it off a solar-cell, like a calculator? Wonder what sorts of untapped benefits it might have, would it be fast? Capable of outputting high-current? High input-voltage tolerance ($V_{ih-max} \gg V^+$, $V_{il-min} \ll V^-$)? Maybe using those base currents that can't be controlled this to drive the one I "discovered" would help in creating output-voltages closer to the rails. Transistors were too leaky and inconsistent performance, binning would be a nightmare. Crossover-distortion? Maybe an inherent hysteresis or dead-zone that



^ v



makes it's noise in /home/0? Or if that doesn't work, let's do it in /tmp/
Esc:ene wrote 01/08/2017 at 11:24
logic better on gaining power when ordering 1M parts
Hah, the idea of a homebrew transistor-CPU running at a 0.8V
(Can you tell the difference between 0.8V and 0.9V? Oh, the
game started, off to be minorly-distracted!)

edit delete

reply edit delete



Yann Guidon / YGDES wrote 01/08/2017 at 12:34

I'd say 1V ? Less than 1.2V anyway. But there is the drop voltage to consider...

Who wants to try it ? :-D



Add your comment

Post comment

↑ Going up?

About Us Contact Hackaday.io Give Feedback Terms of Use Privacy Policy
Hackaday API

© 2017 Hackaday